

TASK 2

REG NO: 23BCE2001


NAME: G.Siddarth

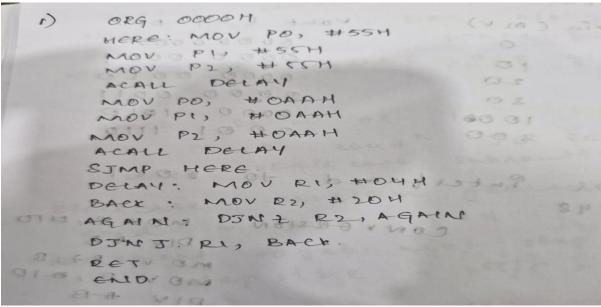Q)Write and assemble a program to toggle all the bits of P0, P1, and P2 continuously by sending 55H and AAH to these ports. Put a time delay between the "on" and "off" states. Then using the simulator, single-step through the program and examine the ports. Do not single-step through the time delay call.




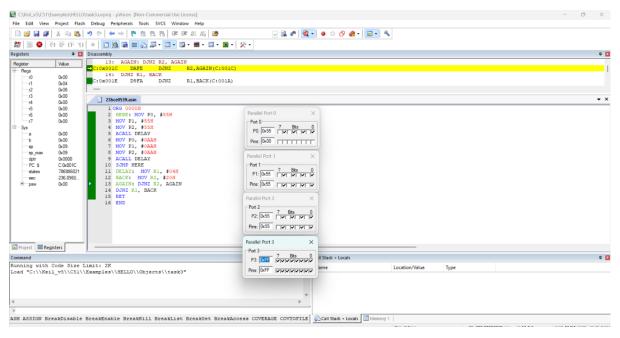


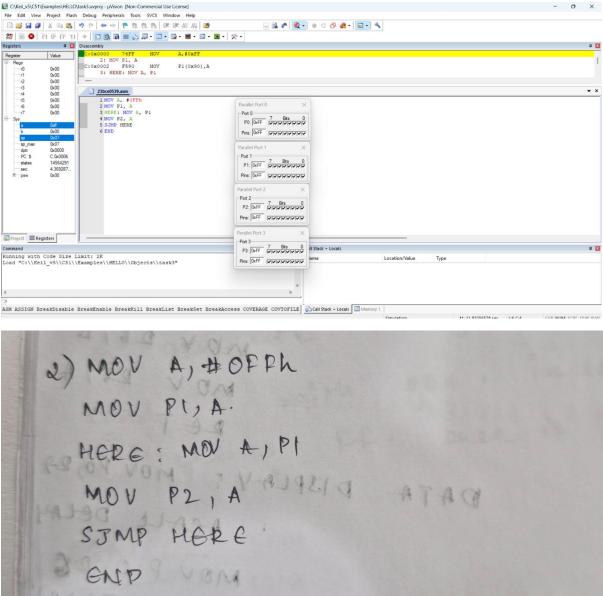
Q)Get the Data from Port P1 and Send it to Port P2, Note: P1 as input Port and P2 as Output Port




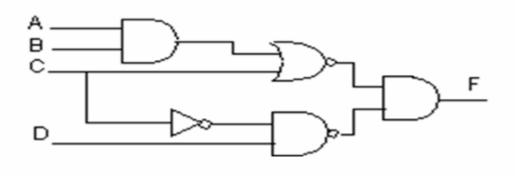Q) Objective: To develop an assembly code for 8051 Microcontroller, to implement the given digital circuit using KEIL development tool



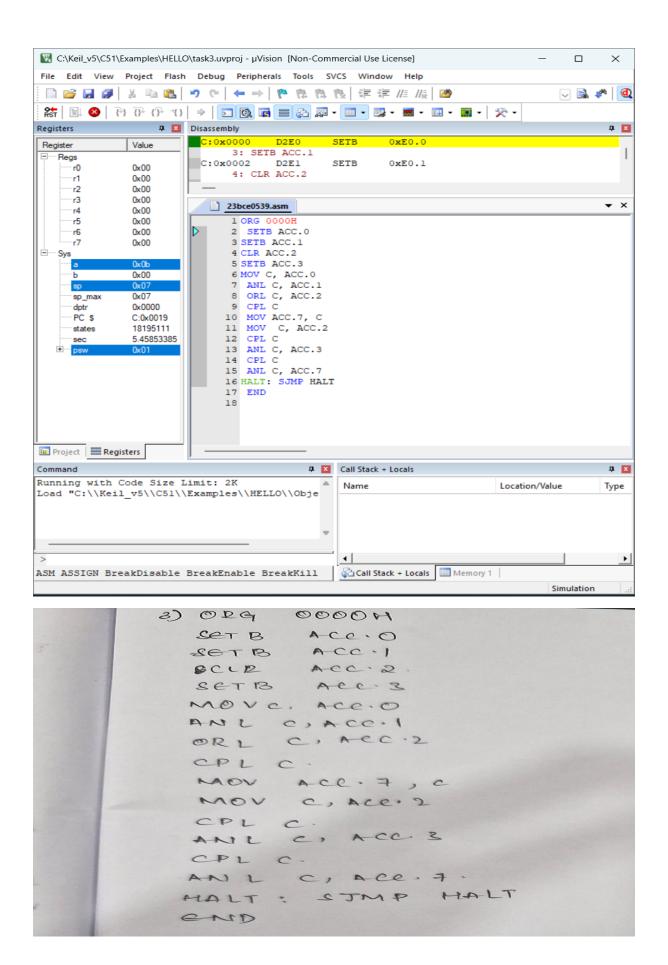

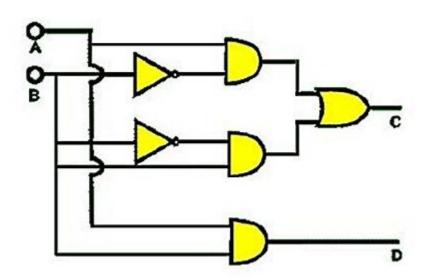

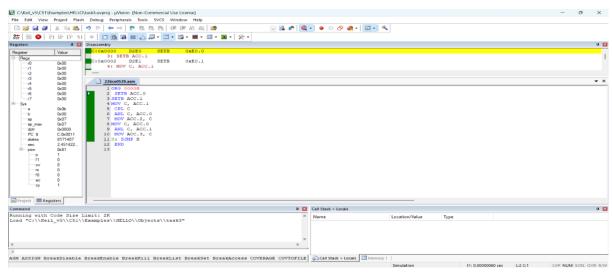

A) ORGODODH

SET B ACC.O

SETB ACC.I

NOV C, ACC.I

CPL C.

ANIL C, ACC.O

NOV ACC. 2, C

MOV C, MCC.O

MOV ACC. 3, C.

M: SJMP H

CRID